

# SMPS-UPS MCQs - Unit 4 and 5

GPT-4-Turbo and Adhithya

May 3, 2024

## 1 UNIT-4 1 mark MCQ

1. What is the primary purpose of using SVPWM in a three-phase inverter?

- A. To increase the output frequency
  - B. To reduce the switching losses
  - C. **To maximize the DC link utilization**
  - D. To simplify the control circuit
- 

2. Which type of multilevel inverter uses capacitors to clamp the voltage to different levels?

- A. Diode clamped
  - B. **Flying capacitor**
  - C. Cascaded H-bridge
  - D. None of the above
- 

3. In sine PWM, the reference signal is typically a:

- A. Square wave
  - B. Sawtooth wave
  - C. **Sine wave**
  - D. Triangle wave
- 

4. Which harmonic elimination technique involves adjusting the switching angles?

- A. SVPWM
  - B. PSPWM
  - C. **ShePWM**
  - D. None of the above
- 

5. A cascaded H-bridge inverter requires which of the following for operation?

- A. **Multiple DC sources**
  - B. A single DC source
  - C. No DC sources
  - D. AC sources
-

6. Which type of inverter is most suitable for high-power applications?

- A. Single-phase inverter
  - B. **Three-phase inverter**
  - C. Both are equally suitable
  - D. Neither is suitable
- 

7. What is a common application of multilevel inverters?

- A. Small household appliances
  - B. High-frequency signal generation
  - C. **Large electric drives and grid interfacing**
  - D. Low power mobile devices
- 

8. PSPWM stands for:

- A. **Phase Shifted Pulse Width Modulation**
  - B. Power Series Pulse Width Modulation
  - C. Pulse Skip Pulse Width Modulation
  - D. None of the above
- 

9. Flying capacitor multilevel inverters are known for:

- A. Their simple structure
  - B. Requirement of many diodes
  - C. **Balancing voltage across various levels**
  - D. High switching frequencies only
- 

10. Which PWM technique is known to produce the least Total Harmonic Distortion (THD)?

- A. Sine PWM
  - B. Modified Sine PWM
  - C. **Space Vector PWM**
  - D. Triangle PWM
- 

11. In a diode clamped inverter, the clamping diodes are used to:

- A. Increase the output voltage
  - B. Reduce the output voltage
  - C. **Clamp the voltage to safe levels**
  - D. Convert AC to DC
- 

12. Which type of filter is most commonly used with PWM inverters?

- A. **Low-pass filter**
- B. High-pass filter
- C. Band-pass filter

D. Band-stop filter

---

13. **The main disadvantage of a single-phase inverter compared to a three-phase inverter is:**

- A. Higher cost
  - B. More complex control
  - C. **Lower power output**
  - D. Higher power output
- 

14. **Which of the following is a feature of multilevel inverters?**

- A. **Lower electromagnetic interference**
  - B. Higher switching losses
  - C. Simpler gate driving circuits
  - D. Fewer output voltage levels
- 

15. **Space Vector PWM improves the inverter performance by:**

- A. Reducing the modulation index
  - B. Increasing the modulation index
  - C. **Optimizing the switching sequence**
  - D. Decreasing the switching frequency
- 

16. **Harmonic elimination in inverters can be achieved by:**

- A. Increasing the frequency of the input DC signal
  - B. Using a single level inverter structure
  - C. **Proper selection of switching angles**
  - D. Decreasing the load resistance
- 

17. **A typical application of cascaded multilevel inverters is:**

- A. Mobile charging
  - B. **Electric vehicle drivetrains**
  - C. Battery charging for low voltage devices
  - D. Small scale residential solar installations
- 

18. **Which technique is used to control the output voltage of inverters by adjusting the duty cycle of the switches?**

- A. Frequency modulation
  - B. Amplitude modulation
  - C. **Pulse-width modulation**
  - D. Phase modulation
- 

19. **The main reason for using multilevel inverters in high power applications is to:**

- A. Reduce the size of the inverter
  - B. **Increase efficiency by reducing switching losses**
  - C. Simplify the control strategy
  - D. Increase the heat dissipation
- 

20. In terms of output quality, multilevel inverters offer:

- A. Higher harmonic content
  - B. **Lower harmonic content**
  - C. Unchanged harmonic content
  - D. None of the above
- 

## 2 UNIT-4 2 mark MCQ

21. In a three-phase inverter using Space Vector PWM, what is the effect of increasing the switching frequency on the output waveform?

- A. Increases the harmonic distortion
  - B. **Reduces the harmonic distortion**
  - C. No change in harmonic distortion but increases efficiency
  - D. Reduces efficiency due to higher switching losses
- 

22. What is a key advantage of using a cascaded H-bridge multilevel inverter with separate DC sources for each H-bridge?

- A. It can utilize higher switching frequencies without significant losses.
  - B. It allows for independent control of each phase.
  - C. It simplifies the overall control system.
  - D. **It enables the use of lower voltage rated components for high voltage applications.**
- 

23. How does the use of a flying capacitor multilevel inverter help in managing the switching stress on semiconductor devices?

- A. **By reducing the voltage across each switch with the help of flying capacitors.**
  - B. By completely eliminating the need for external clamping diodes.
  - C. By allowing higher frequencies to be used without additional cooling.
  - D. By simplifying the gate drive requirements.
- 

24. In the context of harmonic elimination using ShePWM, what is the primary method to determine the optimal switching angles?

- A. Fourier series analysis to minimize specific harmonic orders.
  - B. Trial and error in real-time operations.
  - C. **Use of genetic algorithms or other optimization techniques.**
  - D. Implementing fixed angles based on the number of levels in the inverter.
-

25. What is the primary challenge when implementing SVPWM in a three-phase inverter system?

- A. It requires transformation of three-phase quantities to two-phase quantities.
  - B. The switching losses are significantly higher than other PWM techniques.
  - C. **It is computationally intensive due to the need for real-time calculation of space vectors.**
  - D. It cannot be used with multilevel inverters.
- 

### 3 UNIT-5 1 mark MCQ

26. What is the main purpose of an online UPS?

- A. To provide power during short interruptions
  - B. To condition the power supply
  - C. **To provide backup power without interruption**
  - D. To filter high-frequency noise
- 

27. A voltage filter in a PWM VSI primarily serves to:

- A. Convert DC to AC
  - B. **Reduce the voltage ripple**
  - C. Increase the output voltage amplitude
  - D. Modulate the frequency
- 

28. Which type of UPS provides power to the load only when the mains supply fails?

- A. **Offline UPS**
  - B. Online UPS
  - C. Line-interactive UPS
  - D. None of the above
- 

29. In designing inductors for power electronics applications, which factor is most critical?

- A. Resistance
  - B. Capacitance
  - C. **Inductance**
  - D. Conductance
- 

30. Series-parallel resonant filters are used to:

- A. Increase the efficiency of power conversion
  - B. Minimize the effect of load variations
  - C. Enhance the power factor
  - D. **Suppress specific harmonic frequencies**
- 

31. A DC filter in a power electronic circuit is used to:

- A. Convert AC to DC
  - B. **Smooth out the DC output**
  - C. Increase the DC voltage
  - D. Decrease the DC voltage
- 

32. The primary function of a current filter in a power electronic system is to:

- A. Increase current flow
  - B. Decrease current flow
  - C. **Stabilize current fluctuations**
  - D. Convert AC current to DC current
- 

33. What is a common application of power conditioners?

- A. To charge batteries
  - B. To drive electric motors
  - C. **To improve power quality for sensitive electronics**
  - D. To reduce power consumption
- 

34. The design of a voltage module regulator for electrical drive applications is aimed at:

- A. Reducing the input voltage
  - B. **Stabilizing the output voltage**
  - C. Increasing the efficiency of the motor
  - D. Decreasing the power factor
- 

35. Which UPS feature is critical for data centers requiring high availability?

- A. High power capacity
  - B. Extended battery life
  - C. **Seamless power transfer**
  - D. Low noise operation
- 

36. In power electronics, what is the primary role of filters?

- A. To convert energy
  - B. To store energy
  - C. **To improve the quality of the output signal**
  - D. To regulate voltage
- 

37. Which component is essential for designing an inductor used in power electronic applications?

- A. Diode
- B. Capacitor
- C. **Core material**
- D. Resistor

---

38. What distinguishes an online UPS from an offline UPS?

- A. Online UPS is cheaper
- B. **Online UPS provides continuous power**
- C. Offline UPS uses more energy
- D. Offline UPS has no batteries

---

39. Which type of resonant filter is used to eliminate the need for series capacitors?

- A. Voltage filter
- B. Series-parallel resonant filter
- C. **Filter without series capacitors**
- D. Current filter

---

40. Power line disturbances are primarily dealt with using:

- A. UPS systems
- B. Low-pass filters
- C. **Power conditioners**
- D. Voltage regulators

---

41. What is the main benefit of using an offline UPS for home appliances?

- A. **Cost-effectiveness**
- B. High power output
- C. Continuous power supply
- D. High-speed switching

---

42. The design of transformers for power electronic applications should primarily focus on:

- A. **Minimizing core losses**
- B. Maximizing resistance
- C. Reducing capacitance
- D. Enhancing inductance

---

43. Which filter type is specifically designed to handle the high frequency switching of PWM VSI?

- A. DC filter
- B. Voltage filter
- C. Current filter
- D. **Filter for PWM VSI**

---

44. A major advantage of using series-parallel resonant filters in power conditioners is:

- A. They can operate at very low frequencies

- B. They are less expensive than other filters
  - C. **They offer precise control over the frequency range**
  - D. They require no maintenance
- 

45. **The purpose of designing a voltage module regulator for electrical drive applications is to:**

- A. Increase the torque output
  - B. **Regulate the voltage supplied to the drive**
  - C. Convert AC to DC efficiently
  - D. Reduce electromagnetic interference
- 

## 4 UNIT-5 2 mark MCQ

46. **How does an online UPS differ from a line-interactive UPS in terms of voltage regulation?**

- A. **Online UPS continuously regulates the voltage, whereas line-interactive UPS only adjusts during significant voltage drops or surges.**
  - B. Online UPS uses passive filtering, while line-interactive uses active power conditioning.
  - C. There is no difference; both provide continuous voltage regulation.
  - D. Line-interactive UPS provides better regulation due to the presence of an autotransformer.
- 

47. **In designing a filter for a PWM VSI, what is the main consideration to effectively reduce the output voltage ripple?**

- A. The filter must have a high Q-factor to resonate at the switching frequency.
  - B. The cutoff frequency of the filter must be well below the fundamental frequency of the inverter.
  - C. **The inductance and capacitance values must be chosen to minimize impedance at the fundamental frequency.**
  - D. The filter must be able to handle high power without significant losses.
- 

48. **What is the primary benefit of using a multistage filtering approach in a power electronic system?**

- A. It allows for modular design and easier maintenance.
  - B. **It can target and suppress multiple harmonic frequencies more effectively.**
  - C. It reduces the overall cost of the system by using cheaper components.
  - D. It increases the power handling capacity of each filter stage.
- 

49. **In a power conditioner, what is the impact of non-linear loads on the power quality, and how does the conditioner mitigate this?**

- A. Non-linear loads increase the reactive power; conditioners use capacitors to correct the power factor.
- B. **Non-linear loads introduce harmonics; conditioners use harmonic filters to clean the power.**
- C. Non-linear loads cause voltage sags; conditioners use boost converters to maintain voltage levels.
- D. Non-linear loads lead to frequency variations; conditioners use PLLs to stabilize the frequency.



---

50. Considering the design of transformers for power electronic applications, what specific characteristic is crucial for minimizing energy losses at high frequencies?

- A. High permeability core material
  - B. Low core saturation flux density
  - C. High thermal conductivity of the core
  - D. **Low core loss materials**
-